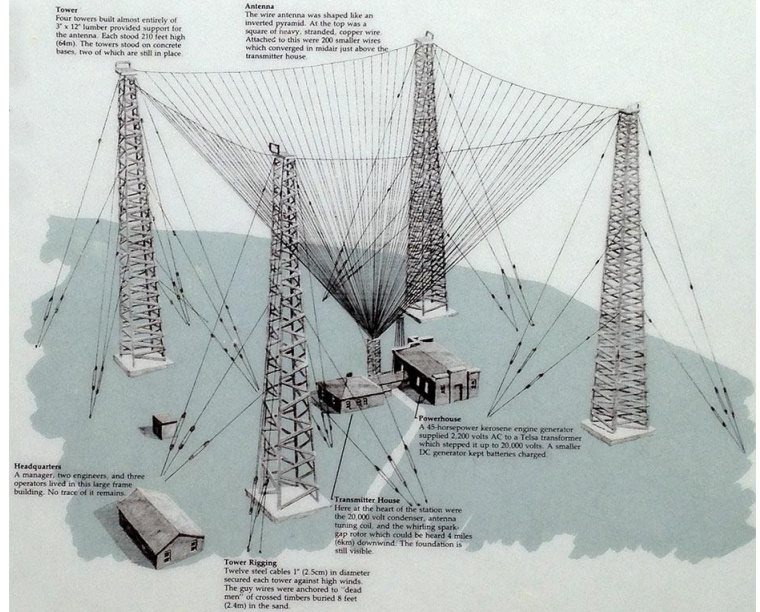


## Marconi Wireless Station

South Wellfleet, Cape Cod, MA

January 18, 1903



# Electronics - PHYS 2371/2



**Calendar of Topics Covered**  
 Physics PHYS 2371/2372, Electronics for Scientists  
 Don Heiman and Hari Kumarakuru  
 Northeastern University, Fall 2020



Also see [Course Description](#) and [Syllabus](#)

This is a schedule of the topics covered, but it may be modified occasionally (08/13/2020).

Week #	Lectures	Weekly Topics (Chs.)	Homework (Ch-Problem)	Lab Experiments (always look for latest version)
I Sept 9-11	<b>Wed Lecture</b> <a href="#">Introduction</a>	Basic Concepts (Ch-2) Ch-16, Digital Multimeters		<a href="#">Worksheet-1,</a> <a href="#">Electronics Introduction</a> (multimeter, voltage sources)
II Sept 16-18	<b>Wed Lecture</b> <a href="#">Electronic Basics</a>	Basic Circuit Analysis (Ch-3) Some Simple Circuits (Ch-4) Resistor/ Capacitor (Ch-47/48)	<a href="#">2-8/9, 3-5/6,</a> <a href="#">4-4/8, 4-</a> <a href="#">13/14</a>	<a href="#">Worksheet-2,</a> <a href="#">Electronic Basics</a>
III Sept 23-25	<b>Wed Lecture</b> <a href="#">Time-Dependent AC Circuits</a>	The Oscilloscope (Ch-17) AC and Elements of Circuits (Ch-7/8) Circuit Analysis (LRC) (Ch-9/12) Resonance (Ch-10)	<a href="#">7-all, 8-3</a> <a href="#">12-all</a>	<a href="#">Worksheet-3,</a> <a href="#">Time-Dependent AC Circuits</a> (R, RC, LRC)
IV Sept 30-Oct 2	<b>Wed Lecture</b> <a href="#">Semiconductor Devices</a>	Solid State Devices (Ch-40) <i>p-n</i> Junction Diodes (Ch-41) Transistors/Circuits (Ch-42-45)	<a href="#">HW Handout</a>	<a href="#">Worksheet-4,</a> <a href="#">Say Hello (and Goodbye) to the Transistor</a>

**Due next Wednesday, Sept 23**


- HW, Chapters 2-4
- Worksheet-2

## TODAY

- ❑ **Quick Review-Basics**
  - DMM meters
- ❑ **Circuit Analysis**
  - Kirchoff's Laws (V,I)
- ❑ **Simple Circuits**
  - reducing complex circuits
  - **VOLTAGE DIVIDER**
  - capacitors

(video break - Tesla)
- ❑ **Lab techniques**
  - collecting data
  - plotting data
  - precision, accuracy, digits
- ❑ **Worksheet-2,**  
**Electronic Basics**


## Review Basics

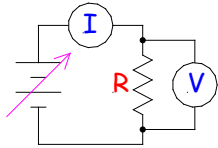

- ❑ **DVM** - digital volt meter
  - high resistance,  $R_{DVM} \gg R$
  - in **PARALLEL** with components
  
- ❑ **DCM** - digital current meter
  - low resistance,  $R_{DCM} \ll R$
  - in **SERIES** with components
  
- ❑ **VERY IMPORTANT !**  $I = V/R$   
When you apply a voltage
  - **resistance determines the current**
  - **you cannot vary both V and I independently**
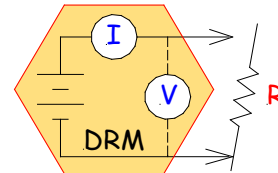
## Multimeters


- ❑ **Ohm Meter** - digital resistance meter
  - applies a **known current**
  - measures the voltage it takes to produce that current
  - uses Ohm's law to compute  $R=V/I$
  
- ❑ **IMPORTANT**
  - remove resistor from circuit
  - current from a circuit must **not** flow thru resistor



## Circuit Analysis
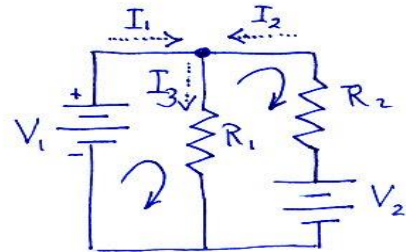
### Kirchhoff's Basic Circuit Laws (Ch. 3)

- ❑ KCL – Kirchhoff's Current Law
- ❑ KVL – Kirchhoff's Voltage Law




## Kirchhoff's Basic Circuit Laws
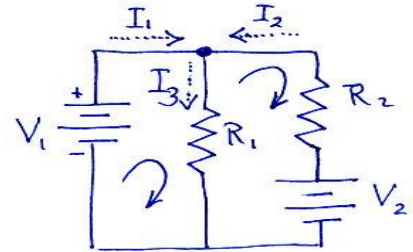
### □ KCL – Kirchhoff's Current Law

$\Sigma I = 0$  at node

Sum of all currents at a point = 0  
*conservation of current or charge*  
 → "what goes in must come out"



### Set up (draw) current arrow

Define the following

- I into node  $I > 0$  ; positive
- I out of node  $I < 0$  ; negative

*Example:*

$$\Sigma I = 0$$

$$I_1 + I_2 - I_3 = 0$$

$$I_1 + I_2 = I_3$$

Note: it's ok that you don't know a priori which direction the current will flow.

After solving the circuit, the currents can have either "+" or "-" signs indicating the true direction.


## Kirchhoff's Basic Circuit Laws

### □ KVL – Kirchhoff's Voltage Law

$\Sigma V = 0$  around **loop**

Voltage must come back to itself around loop  
*"you can't get something for nothing"*

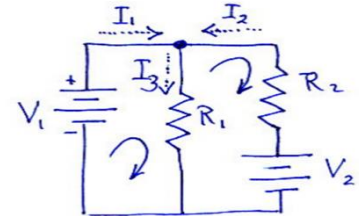- 1) Set up current directions (dotted curves, as before)
- 2) Define **loop** directions (solid curves)
- 3) **Source** – loop arrow out of positive end,  $V > 0$ , positive  
 – loop arrow out of negative end,  $V < 0$ , negative
- 4) **Resistor** – arrows same (current/loop) direction,  $IR < 0$   
 – arrows opposite (current/loop) direction,  $IR > 0$



Note: it's ok if you define the loop direction wrong.

### Example:

Loop-1,	$V_1 - I_3 R_1 = 0$	$\Rightarrow$	$V_1 = I_3 R_1$
Loop-2,	$+I_3 R_1 + I_2 R_2 - V_2 = 0$	$\Rightarrow$	$V_2 = +I_3 R_1 + I_2 R_2$
Substitute	$V_2 = V_1 + I_2 R_2$		
(Large loop)	$V_1 + I_2 R_2 - V_2 = 0$		

## Equivalent Resistance

### □ Series Resistors

around **loop** - use KVL


$$\Sigma V = 0$$

$$V - IR_1 - IR_2 - IR_3 = 0$$

$$V = I (R_1 + R_2 + R_3)$$

$$V = I R_{\text{eff}}$$
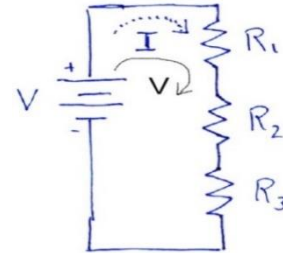
$$R_{\text{eff}} = R_1 + R_2 + R_3 = \Sigma R_i$$



### □ Parallel Resistors

Sum currents at **node** - use KCL

$$\Sigma I = 0 \quad \text{or} \quad I - I_1 - I_2 - I_3 = 0$$

Voltages around loops - use KVL


$$\text{KVL1} \quad V - I_1 R_1 = 0, \quad I_1 = V/R_1$$

$$\text{KVL2} \quad V - I_2 R_2 = 0, \quad I_2 = V/R_2$$

$$\text{KVL3} \quad V - I_3 R_3 = 0, \quad I_3 = V/R_3$$

$$\begin{aligned} I &= V/R_1 + V/R_2 + V/R_3 \\ &= V * (1/R_1 + 1/R_2 + 1/R_3) \\ &= V / R_{\text{eff}} \end{aligned}$$
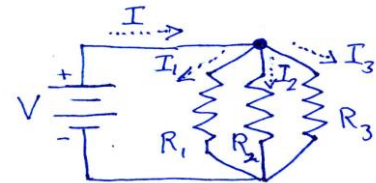
$$1/R_{\text{eff}} = 1/R_1 + 1/R_2 + 1/R_3 = \Sigma (1/R_i)$$



For 2 resistors  
in parallel

$$R_{\text{eff}} = \frac{R_1 R_2}{R_1 + R_2}$$

## Simple Circuit

### Problem 3-7

What is  $I$  for the circuit in Figure 3-15?

$$V_1 = 20 \text{ V}, V_2 = 5 \text{ V}, V_3 = 15 \text{ V}$$

$$R_1 = 100 \ \Omega, R_2 = 25 \ \Omega, R_3 = 250 \ \Omega$$

Apply KVL – no nodes

loop and current in same direction


$$V_1 - IR_3 + V_3 - IR_2 - V_2 - IR_1 = 0$$

$$V_1 + V_3 - V_2 = I (R_3 + R_2 + R_1)$$

$$I = (V_1 + V_3 - V_2) / (R_3 + R_2 + R_1)$$

$$I = (20 \text{ V} + 15 \text{ V} - 5 \text{ V}) / (100 \ \Omega + 25 \ \Omega + 250 \ \Omega)$$
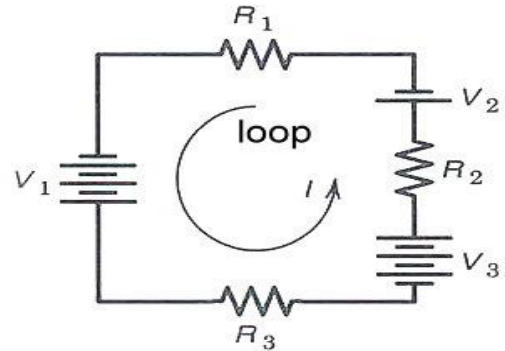
$$\mathbf{I = 30 \text{ V} / 375 \ \Omega = 0.080 \text{ A} = 80 \text{ mA}}$$





## Equivalent Resistor Circuit

### □ Reducing Complex Circuits






$$R_{e1} = 40\Omega * 30\Omega / (40\Omega + 30\Omega) = 1200/70 = 17\Omega$$

$$R_{e2} = 20\Omega + 20\Omega = 40\Omega$$

$$R_{e3} = 17\Omega + 20\Omega = 37\Omega$$

$$R_{e4} = 40\Omega * 37\Omega / (40\Omega + 37\Omega) = 1480/77 = 19\Omega$$
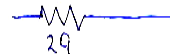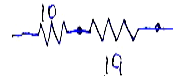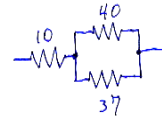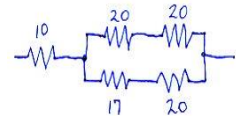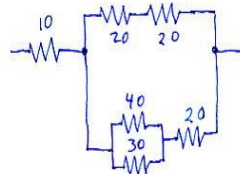
$$R_{total} = 10\Omega + 19\Omega = 29\Omega$$



## Simplifying Circuits

### □ Reducing Complex Circuits


Example: Given  $V=10\text{ V}$ , find the battery current  $I$

$$R_{e1} = (1/3\Omega + 1/2\Omega + 1/1\Omega)^{-1} = 0.55\Omega$$

$$R_{e2} = (1/4.55\Omega + 1/5\Omega)^{-1} = 2.4\Omega$$

$$R_{\text{total}} = 16.4\Omega$$
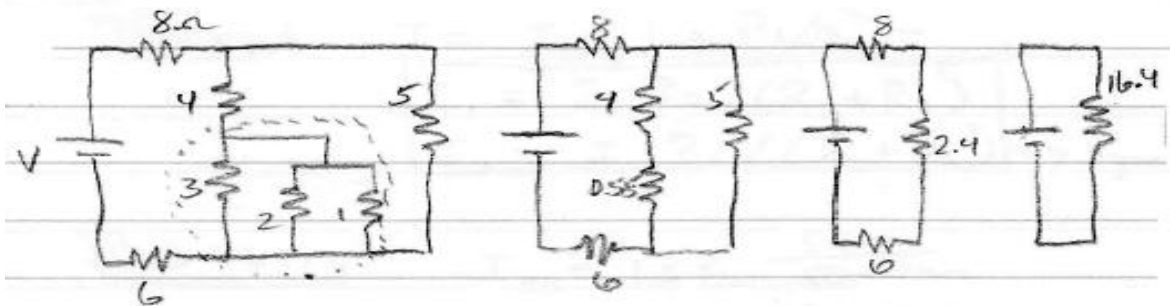
$$I = V / R_{\text{total}} = 10\text{ V} / 16.4\Omega = \mathbf{0.61\text{ A}}$$





## Voltage Divider Equation

KVL1  $V_{in} - IR_1 - IR_2 = 0$   
 $V_{in} = I (R_1 + R_2)$   
 $I = V_{in} / (R_1 + R_2)$

KVL2  $-V_{out} + IR_2 = 0$   
 $V_{out} = IR_2$
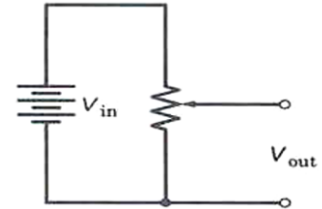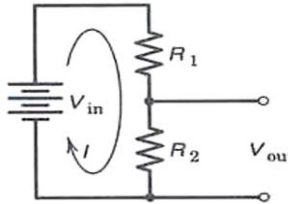
$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$




Imagine a wire with a variable resistance.

### Problem ~4-9



Find the output voltage.

$$V_{out} = 15V \frac{50\Omega}{100\Omega + 50\Omega}$$
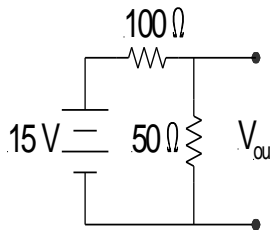
$$= 15V \left( \frac{50\Omega}{150\Omega} \right) = 5V$$






Redraw circuit

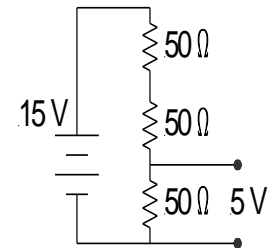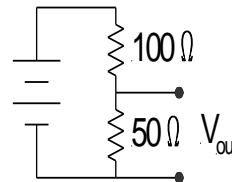
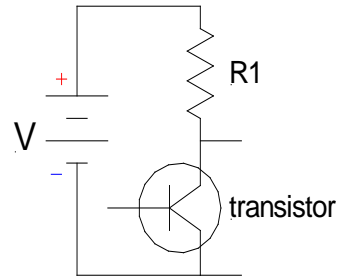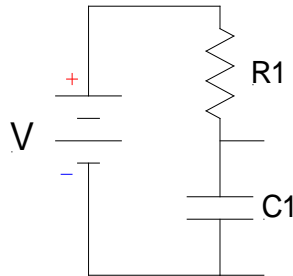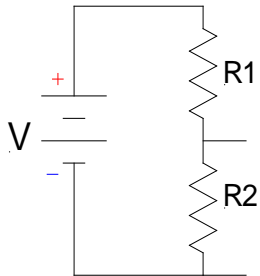
## Voltage Divider with Other Components

You will see voltage dividers many many many times in electronics.



Either R1 or R2 many be replaced by a capacitor, inductor, transistor, etc.


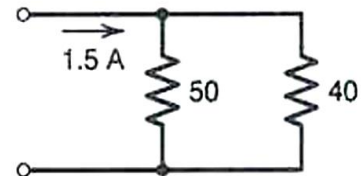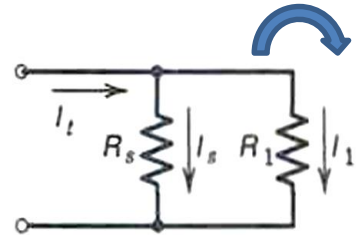
## Current Divider Circuit

KVL  $- I_1 R_1 + I_s R_s = 0$  CW around loop  
 or  $I_s = I_1 R_1 / R_s$

KCL  $I_t = I_s + I_1$  at node  
 $I_t = I_1 R_1 / R_s + I_1$   
 $I_1 = I_t R_s / (R_s + R_1)$   
 $I_s = I_t R_1 / (R_s + R_1)$  by symmetry  
 current divider!



### Problem 4-13

Find the currents.

$$I_{50} = 1.5 \text{ A} * 40 \text{ } \Omega / (50 \text{ } \Omega + 40 \text{ } \Omega)$$

$$= 1.5 \text{ A} * 0.44$$

$$I_{50} = \mathbf{0.67 \text{ A}}$$

$$I_{40} = \mathbf{0.83 \text{ A}}$$

Q: which resistor has the highest current?

## Capacitors

$C = \epsilon A/d$ ; Area, distance between


$$C=Q/V \text{ or } V=Q/C \text{ or } \mathbf{Q = CV}$$

### □ Parallel Capacitors

$$C_{\text{eff}} = \epsilon (A_1 + A_2 + A_3)/d$$



more area
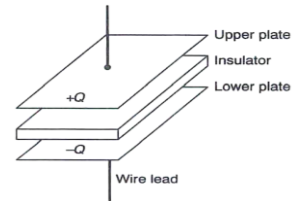
$$\mathbf{C_{\text{eff}} = C_1 + C_2 + C_3 = \Sigma C_i}$$


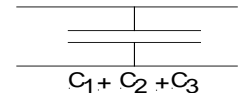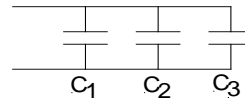
### Field-effect device

Electric field of charge +Q on one plate, forces the opposite charge -Q away from the other plate.



### □ Series Capacitors

$$V_1 = Q_1/C_1, \quad V_2 = Q_2/C_2$$

$$\text{but } \mathbf{Q_1 = Q_2 = Q}$$

$$V_1 = Q/C_1, \quad V_2 = Q/C_2$$

$$V = V_1 + V_2$$


$$= Q/C_1 + Q/C_2$$

$$\text{Also, } V = Q/C_{\text{eff}}$$

$$\text{or } Q/C_{\text{eff}} = Q/C_1 + Q/C_2$$

$$\mathbf{1/C_{\text{eff}} = 1/C_1 + 1/C_2}$$
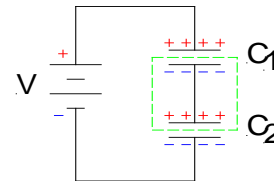
$$\mathbf{C_{\text{eff}} = (\Sigma 1/C_i)^{-1}}$$



**Sum values:** series resistors – parallel capacitors

**Sum reciprocals:** parallel resistors – series capacitors

**Break – Video**

Tesla (0-9:00)

## **Some Experimental Details**



### Accuracy versus Precision

**1. Precision** – how **exact** is a measurement, or how “*fine*” is the scale (# of significant figures).

Suppose you measure a resistor with a digital ohmmeter. The ohmmeter reads 1.53483  $\Omega$ . This number has a high precision. However, it may not represent the “true” resistance as the wires connecting the resistor and ohmmeter have some small resistance that contributes to the measurement.

**2. Accuracy** – how **close** is the measurement to the “**true**” value.

Accuracy is a measure of the *correctness* of the measurement. To determine a more accurate value for the resistor’s resistance, you subtract the resistance of the wires.

## Significant Digits and Round-off

**Rule: round off a computed answer to same number of significant digits as the input number with the smallest number of significant digits.**

Calculators and digital meters produce a much larger number of significant digits than is usually justified. The answer from a calculator has very high *precision*, typically to 8 or 10 digits. In experiments, the number of significant digits is usually much less than this. Suppose you want to divide two values obtained from an experiment – one value has **five** significant digits and the other value has **three**. Although the calculator gives 8 significant digits, the answer is only significant to the smallest number of significant digits, only **three**. You must round-off the calculator number to three significant digits while the fourth significant figure is dropped. When the fourth significant figure is greater than 5, the third significant figure is incremented one unit.

Example:  $V=9.2643 \text{ V}$  and  $I=1.49 \text{ A}$

$$R = 9.2643/1.49 = 6.2176510 \Omega$$

$R = 6.22 \Omega$                       round up the 1 to a 2

It is useful to write numbers in *scientific notation*. For example, the number 0.0000325 would be expressed as  $3.25 \times 10^{-5}$ . When measuring quantities such as voltage, it is best express the values in *engineering notation*, which has powers of 10 in increments of 3. Thus, 0.0000325 volts becomes  $32.5 \times 10^{-6} \text{ V}$ , or **32.5  $\mu\text{V}$** .

## Hints for collecting data

### 1. Take large steps at first

Take 3-5 point up to the maximum.


*e.g.* use  $V=0, 0.3V_{MAX}, 0.6V_{MAX},$  and  $V_{MAX}$

### 2. Plot Data

See where you need to fill in data points.

### 3. Fill in points

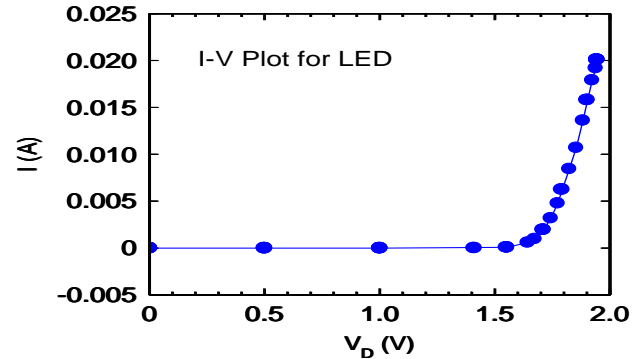- ### 4. Connect points with a curve,
- unless you have a theory curve.



**Worksheet-2, Electronic Basics**

# Electronics - PHYS 2371/2

## DMM

Always use the scale with the most number of digits.



Push **left-most** button that does not show overflow (blinking display).

Gives highest precision and usually a higher accuracy

## Power Supply


1. Make sure the PS is off
2. Turn all 4 knobs counter-clockwise
3. **Turn on PS**
4. Turn up current knob up about one-half
5. Adjust voltage knobs




CCW

off/on  
→

## Protoboard (breadboard) Wiring

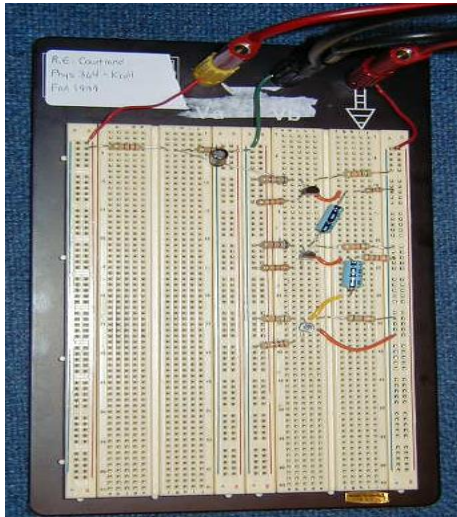

Typical layout with voltage on the red/blue long rows.

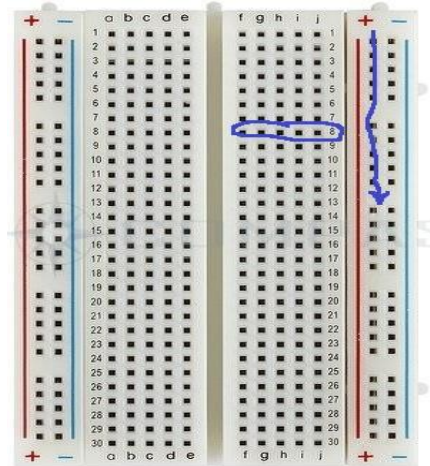

The 5-hole rows are electrically connected horizontally.

The long red/blue rows are connected vertically.

# Electronics - PHYS 2371/2

## Worksheet-2, Electronic Basics

Physics PHYS 2371/2372, Electronics for Scientists  
Don Heiman, Northeastern University

**I. Voltage Divider** – Here, you will investigate *series resistors*.

Note: you will see voltage dividers over and over again in circuits. Most of those will not contain two resistors, but instead may contain a resistor and another component (capacitor, transistor, etc.).

Choose two resistors with different values in the k $\Omega$  range and arrange them in series with the power supply. Next, apply a voltage and measure the voltage across each resistor using the first DMM. Compare the measured voltage ratio to the ratio resistances of resistances.

$$V_{R1}/V_{R2} = \underline{3.42} \quad R_1/R_2 = \underline{3.12}$$

These two resistors in series make a **Voltage Divider**.

**II. Capacitors** – Connect two different capacitors in the 10-100  $\mu\text{F}$  range in series and to the power supply. **Make sure you use the correct polarity on the electrolytic capacitors (longer lead is positive)**. Set up the two DVMs to measure the voltages across each capacitor. Turn on the power supply and measure the voltages quickly after the voltage is applied.

1. Compare your value for voltage ratio to the capacitance ratio.

$$V_{C1}/V_{C2} = \underline{1.62} \quad C_1/C_2 = \underline{0.83}$$

.....

# Electronics - PHYS 2371/2

## I. Voltage Divider – Here, you will investigate *series resistors*.

Note: you will see voltage dividers over and over again in circuits. Most of those will not contain two resistors, but instead may contain a resistor and another component (capacitor, transistor, etc.).

Choose two resistors with different values in the  $k\Omega$  range and arrange them in series with the power supply. Next, apply a voltage and measure the voltage across each resistor using the first DMM. Compare the measured voltage ratio to the ratio resistances of resistances.

$$V_{R1}/V_{R2} = \underline{\hspace{2cm}} \quad R_1/R_2 = \underline{\hspace{2cm}}$$



These two resistors in series make a **Voltage Divider**.

$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$

**II. Capacitors** – Connect two different capacitors in the 10-100  $\mu F$  range in series and to the power supply. **Make sure you use the correct polarity on the electrolytic capacitors (longer lead is positive)**. Set up the two DVMs to measure the voltages across each capacitor. Turn on the power supply and measure the voltages quickly after the voltage is applied.

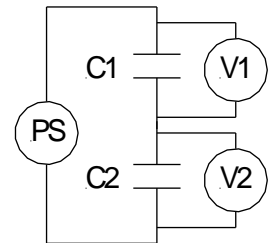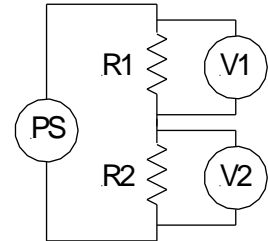1. Compare your value for voltage ratio to the capacitance ratio.

$$V_{C1}/V_{C2} = \underline{\hspace{2cm}} \quad C_1/C_2 = \underline{\hspace{2cm}}$$






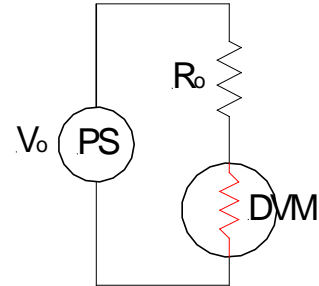**III. Voltmeter Input Impedance** – All voltmeters have an effective resistance, referred to as the *input impedance*. When placed in a circuit, the added resistance of the meter will draw a small amount of current, in effect, changing the circuit. Determine the input impedance of the DVM by using a voltage divider network with the DVM in place of one resistor and use an  $R_o \geq 1 \text{ M}\Omega$  as the other resistor.


If you put a second DVM across  $R_o$ , what effect will that have?

$$V_{DVM} = V_o \frac{R_{DVM}}{R_o + R_{DVM}}$$



## Electronics - PHYS 2371/2

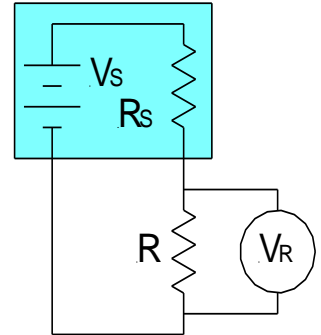**IV. Battery/Power Supply Internal Impedance** – All power sources have a maximum voltage and current that they are capable of producing. For example, leaving the output terminals open produces the maximum voltage, while shorting ( $R \sim 0$ ) the output terminals produces the maximum current. In effect, power sources have an internal resistance that limits the current. Determine the *internal impedance*  $R_s$  of the battery or power supply using a voltage divider network as before, where the source impedance is one resistor and the other is an  $R=10\ \Omega$  ( $P=1\ \text{W}$ ) resistor. Hint: measure the source voltage ( $V_o$ ) by disconnecting the  $10\ \Omega$  resistor.



**Lab Experiments**  
or *“No student left behind”*

**Please ask questions !**

*Fin*