
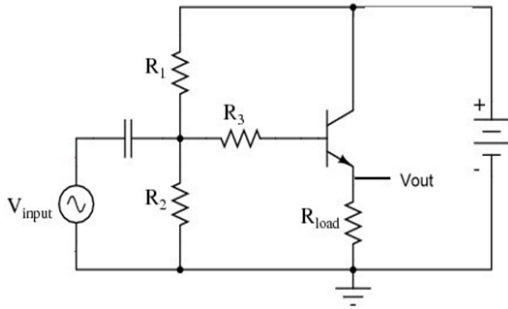


Avoiding Circuit Mistakes

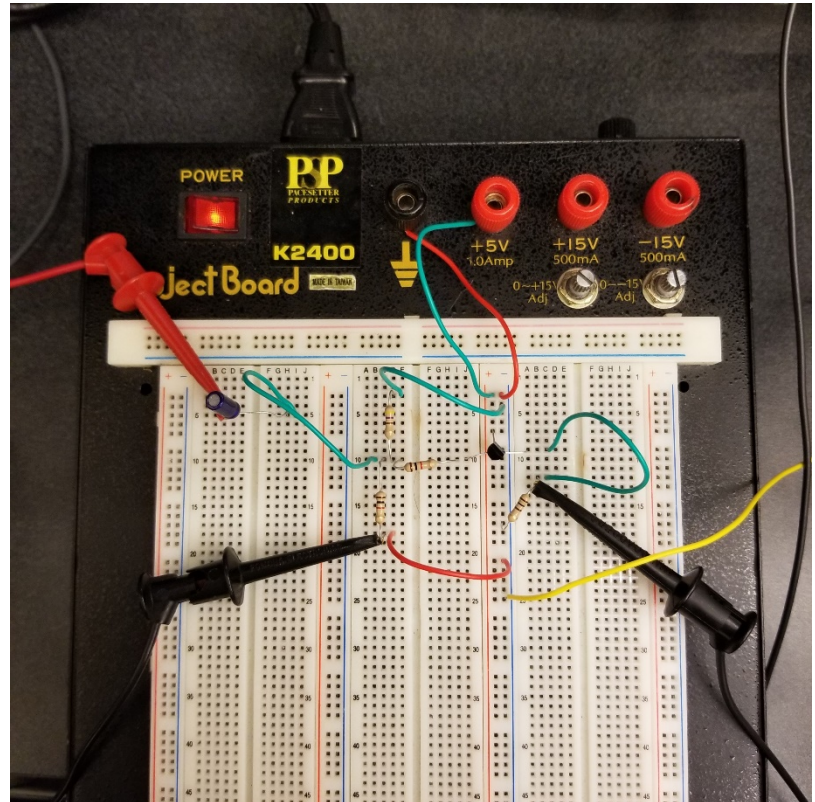

- (1) Does the protoboard circuit look like the circuit diagram?
- (2) Is the wiring simple and easy to troubleshoot?



Review Semiconductors

□ Semiconductors

- Resistivity (ρ), $R = \rho L/A$
a material property
- Si, GaAs, InN, CdTe
 <valence>=4 bonding electrons

□ Doping in Semiconductors

- Donor, *n*-type conduction
 to the right in periodic table
- Acceptor, *p*-type conduction
 to the left in periodic table
- $\rho = 1/ne\mu$, μ =mobility, $\sigma = 1/\rho$


□ pn-Junction Diode

- Depletion Region **narrows** in forward bias
- Depletion Region **widens** in reverse bias

□ Transistors

- 2 diodes
- Bias the base input

II	III	IV	V	VI
	B	C	N	O
	Al	Si	P	S
Zn	Ga	Ge	As	Se
Cd	In	Sn	Sb	Te
Hg				

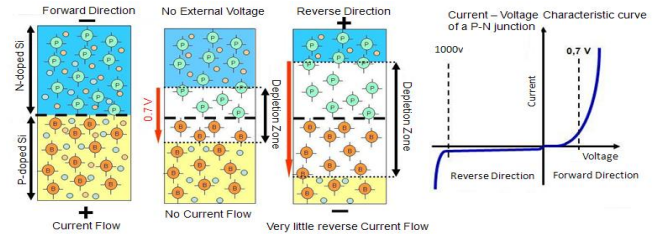

Questions ?

Review Transistors


□ Transistors

- Bipolar Junction Transistor – npn, pnp
- **Base-controlled variable resistor**
- Use as **Voltage Divider** circuit
- Regimes:

cut-off $R \rightarrow$ large

linear $R \rightarrow$ finite

saturated $R \rightarrow$ small

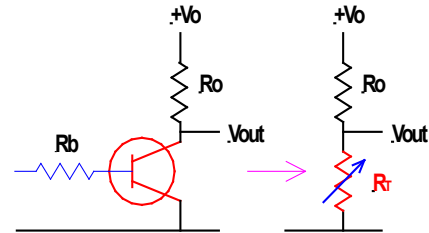

$$V_{OUT} = V_0 \left(\frac{R_T}{R_T + R_0} \right)$$

Any Transistor

- **Base-controlled VARIABLE RESISTOR**
- Use in a **VOLTAGE DIVIDER** circuit

Review Transistors

❑ FET – Field Effect Transistor


$$R = \rho L/A$$

Area changes by electric field via applied voltage

- 99.9999+ % of all transistors

❑ MOSFET - Metal Oxide Semiconductor FET

❑ CMOS - Complementary MOS

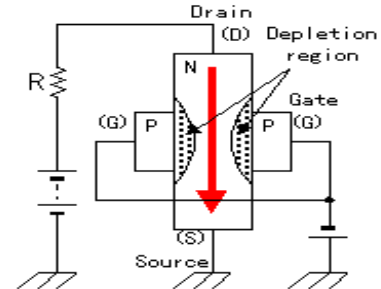


MOSFET

Oxide layer prevents current into the gate

CMOS

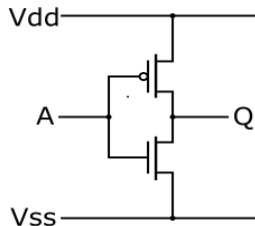One FET is always **off**, the other FET is always on.
No current flows to ground when off.



Questions ?

Electronics - PHYS 2371/2



Calendar of Topics Covered

Physics PHYS 2371/2372, Electronics for Scientists
 Don Heiman and Hari Kumarakuru
 Northeastern University, Fall 2020

Also see [Course Description](#) and [Syllabus](#)



This is a schedule of the topics covered, but it may be modified occasionally (10/02/2020).

Week #	Lectures	Weekly Topics (Chs.)	Homework (Ch-Problem)	Lab Experiments (always look for latest version)
IV Sept 30-Oct 2	Wed Lecture Semicond pdf Semicond video	Solid State Devices (Ch-40) p - n Junction Diodes (Ch-41) Transistors/Circuits (Ch-42-45)	HW Handout	Worksheet-4 Worksheet-4 video <i>Say Hello (and Goodbye) to the Transistor</i>
V Oct 7-9	Wed Lecture Operational Amplifiers	Op-Amp Basics (Ch-28, 31) Basic Op-Amp Circuits (Ch-29)	28-1/3/4, 29-1/2/3/4	Lab-5, Op-Amps
VI Oct 14	Wednesday Study for EXAM-1	Study for EXAM-1 Basics, AC Circuits, Semiconductors, Op-amps		No Lab
VII Oct 19, 21-23 MON/WED	MONDAY EXAM-1	Wed Lecture Magnetolectronics Magnetic induction/flux Transformers (Ch-11)	11-all	Lab-6, Build a Magnetometer


TODAY

Op-Amp Basics, Ch. 28
 Op-Amp Circuits, Ch. 29

- **Why Op-Amps?**
 - Linear amplification
 - Much easier to configure
- **Golden Rules**
 - Simple way to design Gain
- **What can we do with Op-Amps?**
 - Noninverting amplifier
 - Voltage follower
 - Current-to-voltage converter
- **Do Math with Op-amps**
 - Simple summing amplifier
 - Difference amplifier
 - Differentiator
 - Integrator


Electronics - PHYS 2371/2

Amplifier Uses for Op-Amps

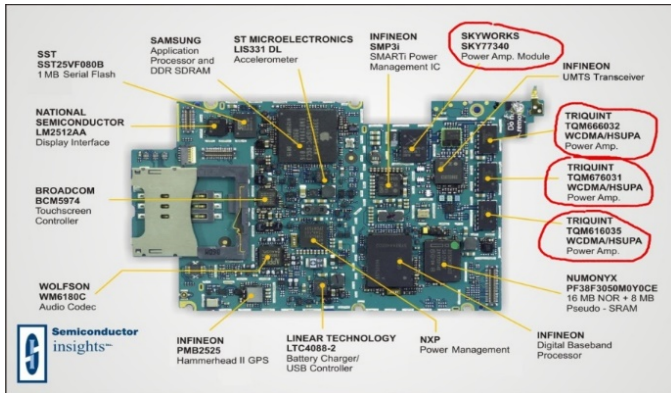

Linear Amplifier

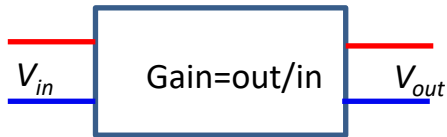
Amplifier
4-terminal device
Negative or positive output



Amplify
Voltage, Current, Power

Voltage Gain
 $G_V \equiv V_{out} / V_{in}$

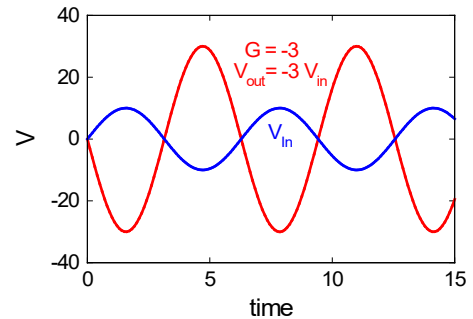- $G_V \gg 1$, e.g. $G_V \sim 10^5$
- $G_V = 1$, unity gain (current gain)
- $0 < G_V < 1$, attenuator
- $G_V < 0$, e.g. $G_V = -3$, inverting



Gain in Decibel Units

Decibels

dB units

Voltage Gain

$$G_V = 10^{\text{dB}/20}$$

$$\text{dB} = 20 \log(G_V)$$

$$\text{Power} = V^2/R$$

Power Gain

$$G_P = 10^{\text{dB}/10}$$

$$\text{dB} = 10 \log(G_P)$$

Voltage Gain

G_V	dB
10^{-2}	-40
1	0
10	20
100	40
1000	60
10^4	80
10^5	100
10^6	120

Power Gain

G_P	dB
10^{-2}	-20
1	0
10	10
100	20
1000	30
10^4	40
10^5	50
10^6	60

Questions ?

History of Operational Amplifiers

Negative feedback

Negative feedback is required for self-regulation or to control the Gain

1927: Negative feedback

Harold Black first developed negative feedback principles as a passenger on the ferry (from Hoboken Terminal to Manhattan) on his way to work at Bell Laboratories. ([see article](#))

1930's: Negative feedback amplifier

Harold Black, Paul Voigt, Alan Blumlein, B.D.H. Telleg




1941: A vacuum tube op-amp

Patented by Karl D. Swartzel Jr. of Bell Labs
Contained [vacuum tubes](#) to achieve a gain of 90 dB
Used in WW II [radar](#) system

1947: An op-amp with an non-inverting input

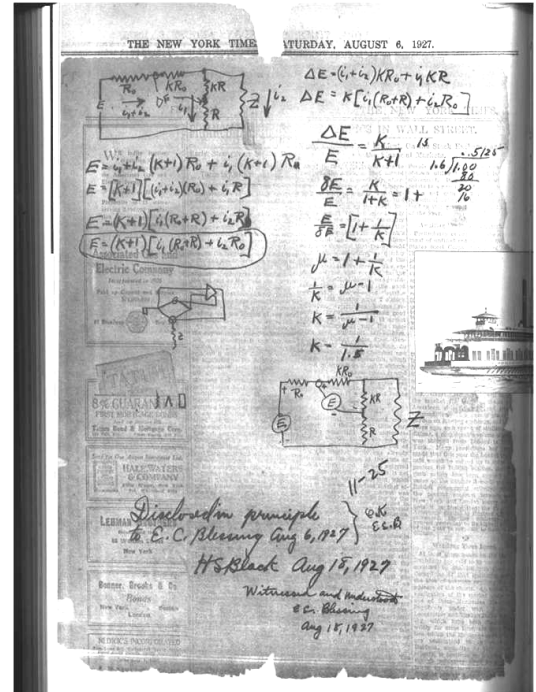First defined in a paper^[15] by John Ragazzini of Columbia U
A footnote mentioned a 2-input op-amp design
by a **student** Loebe Julie.
First op-amp to have inverting and non-inverting inputs.



Op Amp or Op-amp

Two inputs


Noninverting (+)

Inverting (-)

As V_{in} increases

Noninverting: V_{out} **increases**

Inverting: V_{out} **decreases**

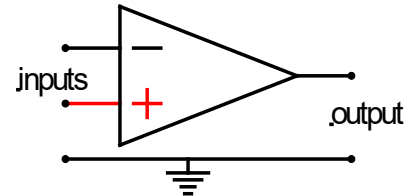

Differential Inputs

V_{out} goes **positive** or **negative**

$$V_{out} = G (|V_+| - |V_-|)$$

For $V_+ > V_-$, $V_{out} > 0$ (pos)

For $V_+ < V_-$, $V_{out} < 0$ (neg)

Example, $G=10$

If $V_- = 1 \text{ V}$, $V_+ = 0 \text{ V}$

$$V_- > V_+$$

then $V_{out} = -10 \text{ V}$

If $V_- = 0 \text{ V}$, $V_+ = 1 \text{ V}$

$$V_+ > V_-$$



then $V_{out} = +10 \text{ V}$

Questions ?

Power Supply for Op-Amp

Dual Supply

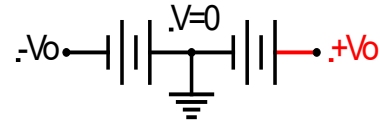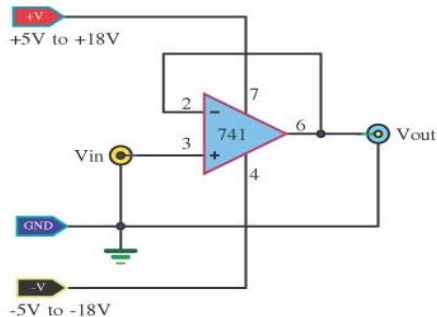Needs a dual voltage supply
 $+V_o$ and $-V_o$ (also called V_{cc})



The power supply is usually not shown in the circuit

Cannot get more V_{out} than the power supply V_o

Example, $G = 10^5$

$$V_- = 1 \text{ V}, \quad V_+ = 0 \text{ V}$$

$$V_{out} \sim -V_o \text{ (supply voltage)}$$

$$V_- = 0 \text{ V}, \quad V_+ = 1 \text{ V}$$

$$V_{out} \sim +V_o \text{ (supply voltage)}$$

Questions ?


Simple Circuit: **Ideal inverting amplifier**

R_f = feedback resistor

- puts part of the output on inverting (-) input

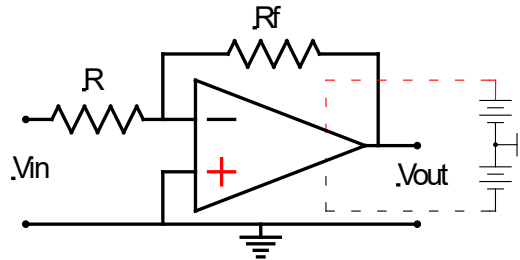Question: What happens if you put part of the output on the noninverting (+) input? (positive feedback)

Answer: output saturates to maximum voltage
(like a microphone in front of a speaker)





Compute Op-Amp Circuit Gain

Golden Rules

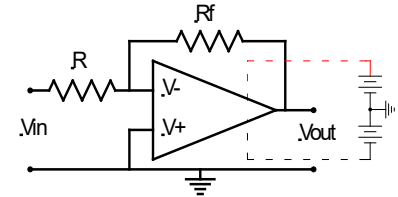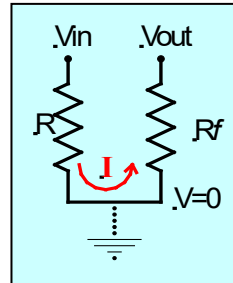1. Assume **op-amp input voltages are equal**
- Virtual Ground Approximation
2. Assume **no current flows into op-amp inputs**
- Infinite Impedance Approximation

Op-amps are designed so that the output adjusts **automatically** to make the 2 op-amp input voltages equal.



Note:

Current is toward $V=0$ for R
Current is away from $V=0$ for R_f

This gives V_{in} and V_{out} **opposite signs** and **G is negative**.

Apply Rule-1 : if $V_+ = 0$ then $V_- = V_+ = 0$ (at ground)

Apply Rule-2 : No currents flow into op-amp (ground)

$$I_R = I_{R_f} = I \quad \text{assume current CCW}$$

Now, $V_{in} = I_R R$ assume V_{in} is positive
and $V_{out} = -I_{R_f} R_f$ since I direction is reversed

$$I = V_{in}/R = -V_{out}/R_f$$

$$\text{so } V_{out} = -V_{in} (R_f/R)$$


$$\text{and Gain} = V_{out}/V_{in} \quad \rightarrow \quad \mathbf{G_o = - R_f / R}$$

[Basics of Opamp circuits \(0-2:50\)](#)

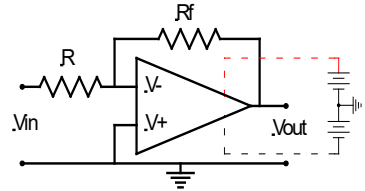Questions ?

Nominal versus Real Op-Amp Gain

- **Nominal** Gain, G_o , from Golden Rules
- **Real** Gain, G , is what the circuit provides
- **Open loop** Gain, A , what the op-amp can provide



$$G_o = -R_f/R \quad \text{nominal gain}$$

$$G = \left(\frac{-R_f}{R} \right) \frac{A}{A + (R_f/R) + 1} \quad \text{real gain}$$

$$A = \text{open loop gain } (\sim 10^5)$$

Prob. 28-2

Given $R=10 \text{ k}\Omega$ and $R_f=1 \text{ M}\Omega$,
compute nominal gain G_o , real gain G and error
for open loop gains of $A=10, 10^3$, and 10^6 .

Use $G_o = -R_f/R$ as nominal or closed loop gain.

$$G_o = -1 \text{ M}\Omega/10 \text{ k}\Omega = \mathbf{-100 \text{ nominal gain}}$$

$$\text{Real gain is } G = G_o A / (A + (R_f/R) + 1)$$

Real gain divided by nominal gain

$$\text{For } A = 10, \quad G/G_o = 10/(10+100+1) = \mathbf{10/111}$$

$$\text{For } A = 10^3, \quad G/G_o = 10^3/(10^3+100+1) = \mathbf{1000/1101}$$

$$\text{For } A = 10^6, \quad G/G_o = 10^6/(10^6+100+1) = \mathbf{1,000,000/1,000,101}$$

$$\text{Error} = 100\% [(G - G_o)/G_o] = 100\% [G/G_o - 1]$$

741 Op-Amp Device Characteristics

~ skip

Open Loop Gain $A_V = 10^5$, 100 db

$$V_{out} = A \Delta V = A (V_+ - V_-) \quad \rightarrow$$

Input Impedance (draws some current)

741 $\sim 2 \text{ M}\Omega$

FET op-amp $\sim 10^{12} \Omega$




Input Offset Voltage (741 has $V_{offset} \sim 2 \text{ mV}$)

$$\text{Gives } V_{out} \leq G * V_{offset} \quad \rightarrow$$

Input Bias Current (741 $\sim 0.1 \mu\text{A}$)

Output Impedance (741, $R \sim 75 \Omega$, 20 mA) \rightarrow

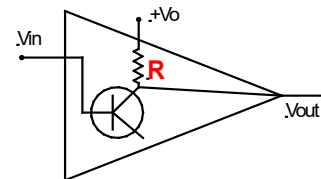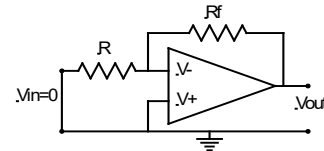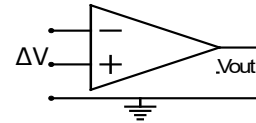Slew Rate = $dV/dt]_{max}$ (741, $\sim \frac{1}{2} \text{ V}/\mu\text{s}$)
How fast V_{out} can be changed




741 Frequency Response

Gain-Bandwidth Product

$$G * f_{\max} = \text{constant} \\ = 10^6 \text{ Hz}$$

If gain is large,
cannot amplify high f .

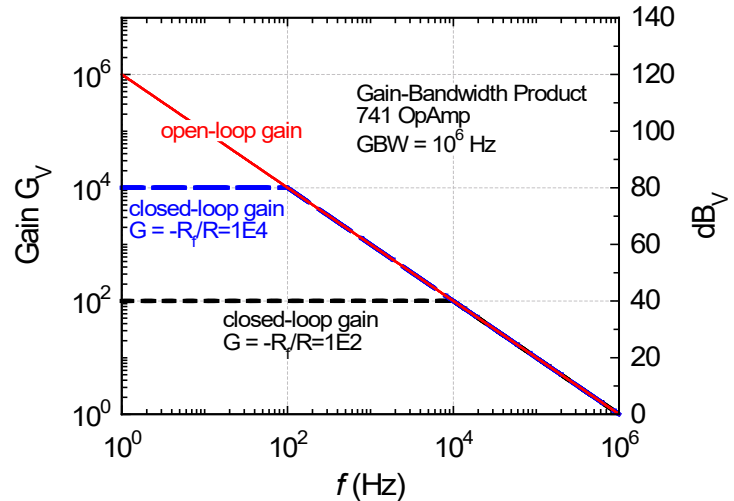If you want high f ,
need to keep gain low.



Questions ?

Things you can do with an Op Amp

Better Inverting Amplifier

Noninverting Amplifier

Voltage Follower

Current-to-voltage Converter

Simple Summing Amplifier

Difference Amplifier

Differentiator

Integrator

skip

Better Inverting Amplifier

Noninverting Amplifier

Voltage Follower

Current-to-voltage Converter


Simple Summing Amplifier

Difference Amplifier

Differentiator

Integrator

**Eliminate
input bias current**

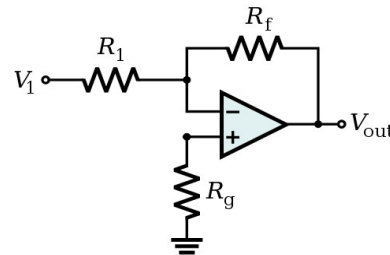

$$G = -R_f / R_1$$

$$\frac{1}{R_g} = \left(\frac{1}{R_f} + \frac{1}{R_1 + R_{source}} \right)$$

Better Inverting Amplifier

Noninverting Amplifier

Voltage Follower


Current-to-voltage Converter

Simple Summing Amplifier


Difference Amplifier

Differentiator

Integrator

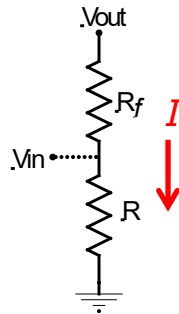

**Positive in
Positive out**

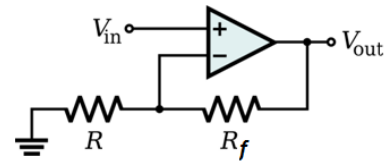

$$I_{R_f} = I_R = I, \quad \text{since } I_- = 0$$

$$V_{in} = IR, \quad \text{since } V_{in} = V_- = IR$$

$$V_{out} - V_{in} = IR_f$$

$$V_{out} = V_{in} + V_{in} (R_f / R)$$

$$G = V_{out} / V_{in} = R_f / R + 1$$

skip

Better Inverting Amplifier

Noninverting Amplifier

Voltage Follower

Current-to-voltage Converter


Simple Summing Amplifier

Difference Amplifier

Differentiator

Integrator

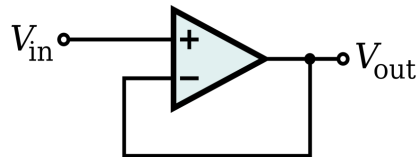Unity gain
Buffer (current) amplifier
High Z_{in} , Low Z_{out}



High Z_{in} implies
low current
($I_{in} \sim V/Z_{in}$)

Low Z_{out} implies
high current
($I_{out} \sim V/Z_{out}$)

$$V_{in} = V_+$$
$$V_{out} = V_-$$
$$V_{in} = V_{out}$$

$G = 1$

skip

Better Inverting Amplifier

Noninverting Amplifier

Voltage Follower

Current-to-voltage Converter


Simple Summing Amplifier

Difference Amplifier

Differentiator

Integrator

**Current In
Voltage Out**

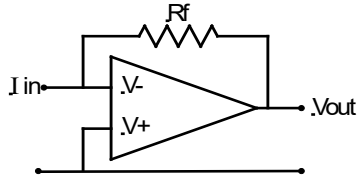

$$V_+ = 0, \quad V_- = V_+$$
$$I_{in} = I_{Rf}$$
$$\mathbf{V_{out} = -I_{in} R_f}$$

Better Inverting Amplifier

Noninverting Amplifier

Voltage Follower

Current-to-voltage Converter

Inverting **Summing** Amplifier

Difference Amplifier

Differentiator

Integrator

Use Op-amps

to do **MATH !**

They can even do
calculus

Add voltages

Better Inverting Amplifier

Noninverting Amplifier

Voltage Follower



Current-to-voltage Converter

Inverting Summing Amplifier

Difference Amplifier

Differentiator

Integrator

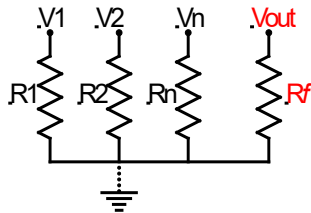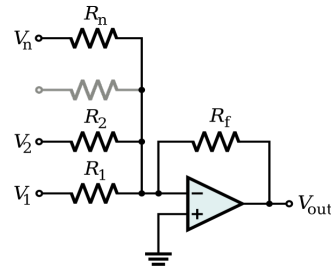


$$V_{out} = -\frac{R_f}{R_1}V_1 - \frac{R_f}{R_2}V_2 \dots - \frac{R_f}{R_n}V_n$$

For $R_1 = R_2 \dots = R_n = R$

$$V_{out} = -\frac{R_f}{R}(V_1 + V_2 \dots + V_n)$$

skip

“Differential Amplifier”

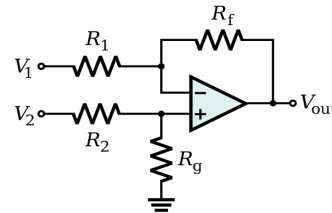

Better Inverting Amplifier

Noninverting Amplifier

Voltage Follower

Current-to-voltage Converter

Simple Summing Amplifier

Difference Amplifier

Differentiator

Integrator

Read Wikipedia

for $R_1 \neq R_2$ and $R_g \neq R_f$

http://en.wikipedia.org/wiki/Operational_amplifier_applications

$$I_+ = I_- = 0, \quad V_+ = V_-$$

$$\text{For } R_1 = R_2 = R, \quad R_g = R_f$$

$$V_+ = V_2 \frac{R_f}{R + R_f}$$

$$\frac{V_{out} - V_-}{R_f} = I_{Rf} = I_{R1} = \frac{V_- - V_1}{R_1}$$


Let $V_- = V_+$ and substitute for V_+

$$V_{out} = \frac{R_f}{R} (V_2 - V_1)$$

Time-derivative of Voltage

dV_{in}/dt

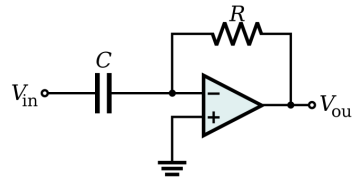- Better Inverting Amplifier
- Noninverting Amplifier
- Voltage Follower
- Current-to-voltage Converter
- Simple Summing Amplifier
- Difference Amplifier
- Differentiator** (inverting)
- Integrator



$$V_{out} = -RC \frac{dV_{in}}{dt}$$

$$V_{out} = -\tau \frac{dV_{in}}{dt}$$

$$V_+ = 0, \text{ since grounded}$$

$$V_- = V_+ = 0$$

$$I_R = I_C = I, \text{ since } I_- = 0$$


$$C = Q / V \text{ or } Q = CV$$

$$I_C = \frac{dQ}{dt} = C \frac{dV_{in}}{dt}$$

$$I_R = -V_{out} / R = C \frac{dV_{in}}{dt}$$

Again $\tau = RC$
units of time (s)

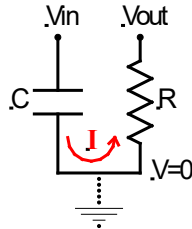For a sine wave
 $\langle G \rangle = \omega \tau$





Questions ?

Time-integration of Voltage

$$\int V_{in} dt$$

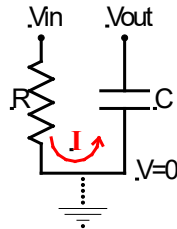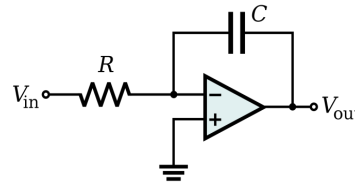- Better Inverting Amplifier
- Noninverting Amplifier
- Voltage Follower
- Current-to-voltage Converter
- Simple Summing Amplifier
- Difference Amplifier
- Differentiator
- Integrator** (inverting)



$$V_- = V_+ = 0 \text{ since grounded}$$

$$I_C = I_R = I \text{ since } I_- = 0$$

$$V_{in} = IR$$

$$Q = CV_{out}, I = \frac{dQ}{dt} = -C \frac{dV_{out}}{dt}$$

$$I = V_{in} / R = -C \frac{dV_{out}}{dt}$$

$$\int \left[\frac{1}{RC} V_{in} = - \frac{dV_{out}}{dt} \right] dt$$

$$V_{out} = - \frac{1}{RC} \int_0^t V_{in} dt$$

$$V_{out} = - \frac{1}{\tau} \int_0^t V_{in} dt$$


Again $\tau = RC$
units of time (s)

For a sine wave
 $\langle G \rangle = 1/\omega\tau$

Questions ?

Homework Example (Ch. 29)

Given the circuit, write the equation.

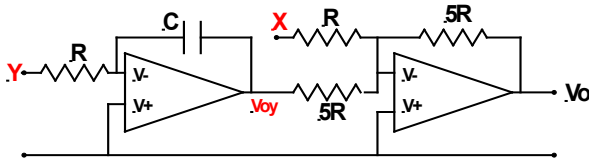

Begin with the voltages **X** and **Y**.

The output voltage from the right hand op-amp is

$$V_{oX} = XG_X = X\left(-\frac{R_f}{R}\right) = X\left(-\frac{5R}{R}\right) = -5X.$$

The left hand op-amp is in an integrator circuit,

$$\text{so } V_{out} = -\frac{1}{RC} \int V_{in} dt \text{ for that op-amp.}$$

Then at point $V_{oY} = -\frac{1}{RC} \int Y dt$, where Y is the input voltage.

V_{oY} is then input in the right hand op-amp,




$$\text{so } V_{oY} \text{ is multiplied by the right hand gain } G = -\frac{5R}{5R} = -1$$

$$\text{to give } \left(-\frac{1}{RC} \int Y dt\right)(-1) = \frac{1}{RC} \int Y dt.$$

$$\text{The total output is now } V_o = -5X + \frac{1}{RC} \int Y dt$$

Questions ?

Homework Example, Ch. 29

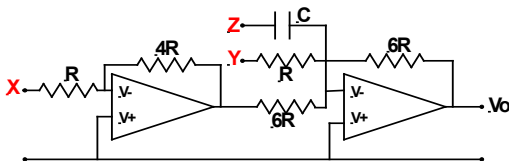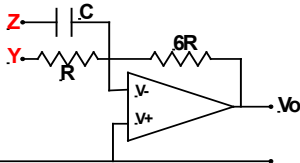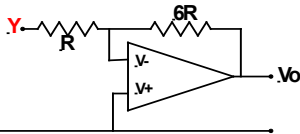

Given the equation, draw the op-amp circuit.

The given output voltage is $V_o = +4X - 6Y - 3 \frac{dZ}{dt}$.

X, Y and Z are voltages

Begin with the voltage Y since that term is negative.

Draw an inverting amplifier with $G_v = -6$, using R and $R_f = 6R$.

You need a differentiating circuit for Z,

so add a capacitor C to the input of that op-amp.

For a differentiator $V_{out} = -RC \frac{dV_{in}}{dt}$.

You need an output of $-3 \frac{dZ}{dt}$,

and since $R_f = 6R$, then $6RC = 3$ or $C = \frac{1}{2R}$.

Finally, you need a $4X$ output.

Add a second op-amp to the left with $G_{1X} = -4$, using R and $R_f = 4R$.

Output this $V = -4X$ into the right hand inverting op-amp

with $G_{2X} = -1 = -\frac{6R}{6R}$.

Thus the output from X is $V_{oX} = G_{1X}G_{2X} = (-4X)(-1) = +4X$.

Questions ?

Lab Experiment – 5

Op-Amp and Circuits


Don't forget to power the chip with
+12 V and -12 V or
+15 V and -15 V

Use the **power supply ground**
as the ground for the
input (V_+ or V_-) and the output (V_{out}).


**We are here to help
Please**

- **ask lots of questions in the lab**
- **come to Zoom on Monday**
- **email questions to TA or me**


Protoboard (breadboard) Wiring

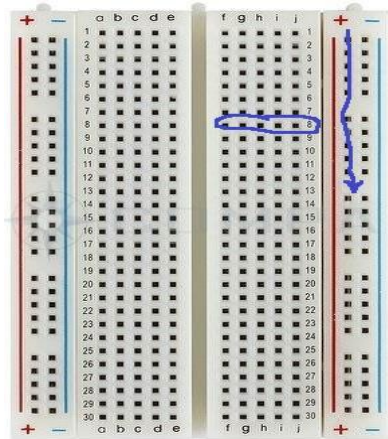

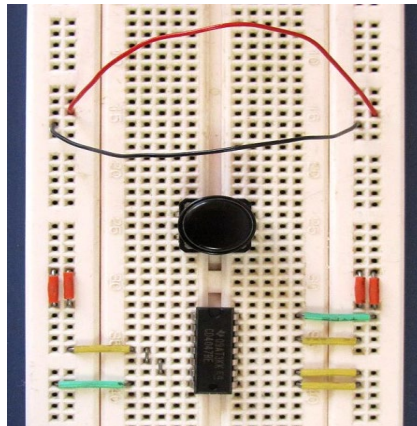The 5-hole rows are connected horizontally.
The long red/blue rows are connected vertically.



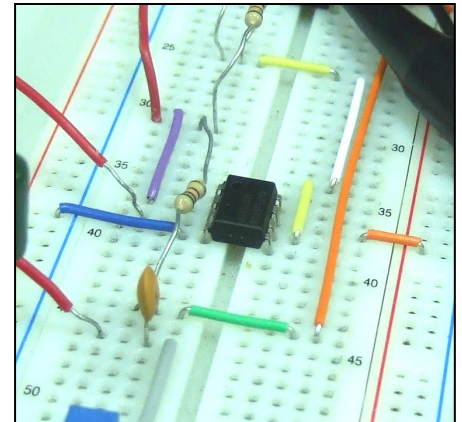Typical layout with voltage
on the long vertical rows.



741 op-amp circuit

Electronics - PHYS 2371/2

Lab-5, Op-Amps and Circuits

Physics PHYS 2371/2372, Electronics for Scientists

Don Heiman and Hari Kumarakuru, Northeastern University

I. Op-amp Basics

Connect $+V_o$, $-V_o$ ($\sim \pm 15$ V) to power the 741. Don't mistake the power supply voltages ($+V_o$ and $-V_o$) with the inputs denoted as V_+ and V_- in textbooks.

1. What is V_{out} when +5 V is applied to the inverting input?
2. What is V_{out} when +5 V is applied to noninverting input?
3. Why does the output voltage saturate near the supply voltages?
4. What is the maximum output current that the 741 can supply?
5. What is the maximum power a 741 can deliver to an 8Ω speaker?

II. Frequency Dependence

III. Differentiator Circuit

IV. Integrator Circuit

V. Summary

Written Lab Report is required.
See the report [Template](#).

Please

- read the instructions before the lab
- visit the Monday discussion section

종료