

Wednesday EXAM-2, Nov 18

Magneto-electronics
Optoelectronics
Digital Electronics
Pulsed ICs

Due Wed, Nov 18

Homework Ch. 21
Lab-8a and 8b in **one report**

Review Digital Circuits

Inside Computers

Very large-scale integration (VLSI)
CPU, central processing unit
> 10^9 transistors (Minecraft computer)

Truth Table

Output for each minterm (=1)

- Karnaugh Map** (simplification $\rightarrow \rightarrow \rightarrow$)
graphical matrix solution
combine groups of minterms (yellow)
wrap around sides to combine (blue)
use minterm more than once (orange)

Truth Table

Row	A	B	C	D	Out
1	1	1	1	1	0
2	1	1	1	0	0
3	1	1	0	1	1
4	1	1	0	0	0
5	1	0	1	1	1
6	1	0	1	0	0
7	1	0	0	1	1
8	1	0	0	0	1
9	0	1	1	1	0
10	0	1	1	0	0
11	0	1	0	1	0
12	0	1	0	0	0
13	0	0	1	1	0
14	0	0	1	0	0
15	0	0	0	1	0
16	0	0	0	0	1

Karnaugh Map Rules

RULE-1: Order top/side table axes, vary only one bit when moving to next cell

RULE-2: group even numbers of "1"s that are adjacent
(You can wrap around the cylinder, as in $AB=10 \rightarrow CD=00$)

RULE-3: Each group is one minterm

RULE-4: If input is both "0" and "1" you don't need that input

Truth Table


AB	00	01	11	10
CD				
00	1	0	0	1
01	0	0	1	1
11	0	0	0	1
10	0	0	0	0

K-map
Simplification



5 & 6-variable K-map

Electronics - PHYS 2371/2

 

Don

Calendar of Topics Covered

Physics PHYS 2371/2372, Electronics for Scientists

Don Heiman and Hari Kumarakuru
Northeastern University, Fall 2020

Also see [Course Description](#) and [Syllabus](#)



Hari

This is a schedule of the topics covered, but it may be modified occasionally (11/07/2020).

Week #	Lectures	Weekly Topics (Chs.)	Homework (Ch-Problem)	Lab Experiments (always look for latest version)
VII Oct 19, 21-23 MON/WED	MONDAY EXAM-I	Wed Lecture Magnetolectronics Magnetolectronics Lecture Magnetic induction/flux Transformers (Ch-11)	11-all	Lab-6, Build a Magnetometer Lab-6 video , Lab-6 data
VIII Oct 28-30	Wed Lecture Optoelectronics Optoele Lecture	<i>Photodiode, LED, laser</i>	none	Lab-7, Optoelectronics (coupled LED-photodiode) Lab-7 Optoele video
IX Nov 2, 4-6 MON/WED	MON Digital-1 Digital-1 video WED Digital-2 Digital-2 Lecture	Mon/Wed Lectures Digital Logic (Ch-19,22), Binary Numbers (Ch-54) Logical Networks (Ch-20)	19-all, 20-all	Lab-8a, Digital Circuits (truth table, 4-bit decoder) Lab-8a Digital video Lab-8a video
X Nov 11-13	Monday Lecture Pulsed ICs Pulsed Lecture	Lecture: Pulsed ICs Digital Summary	21-1/2	Lab-8b, Pulsed Digital (Flip-flops, counter, displays) Lab-8b Pulsed video
XI Nov 18-20 WED EXAM	EXAM-II - Wed Final Project	EXAM-II: Magnetolectronics, Optoelectronics, Digital/Pulsed		Final Project
XII Nov 25-27	No Lecture	Thanksgiving		No Lab
XIII Dec 2	Wed Lecture	Future Electronics		Project PowerPoint due Monday Dec 2 (EG361 or email file)
XIV Dec 7-9	No Classes			

Pulsed Digital Circuits

- **Moore's Law**
- growth of technology
- **Clock Speed**
- **Flip-flops**
- RS flip-flop
- clocked FF
- JK flip-flop
- **Lab-8b**
- Digital Counter

Keyboard → Computer → Monitor

What happens when you press a key on the keyboard?



Key press sends an ASCII code to the computer.
ASCII Code is a number 0-255

Keyboard effectively sends:

- numbers for **math**
- characters for **word processing**
- special characters for **functions**

The computer central processing unit (CPU)

- converts the ASCII code to **binary** numbers (e.g. 10110...)
- uses machine code and assembly language to process the information (**add/multiply/spell check...**)

The memory (ROM/RAM/NonVolatile) stores the information

The graphics card (GPU) converts the information for the monitor

The information from the graphics card (GPU)

- converts the information to **pixels** to display on the **LCD/LEDs** in the monitor.

ANY COMPUTER

All information is coded in **NUMBERS**.
These numbers can be converted to text, symbols or images.

ASCII Keyboard, Hexadecimal

Keyboard uses 8-bits bytes (two 4-bit numbers).
This requires **Hexadecimal** numbers.

Deci	Hexa
0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	8
9	9
10	A
11	B
12	C
13	D
14	E
15	F

Esc	F1	F2	F3	F4	F5	F6	F7	F8	F9	F10	F11	F12		
1B (1B) <1B> Π	0,3B (0,54) <0,5E> [0,68]	0,3C (0,55) <0,5F> [0,69]	0,3D (0,56) <0,60> [0,6A]	0,3E (0,57) <0,61> [0,6B]	0,3F (0,58) <0,62> [0,6C]	0,40 (0,59) <0,63> [0,6D]	0,41 (0,5A) <0,64> [0,6E]	0,42 (0,5B) <0,65> [0,6F]	0,43 (0,5C) <0,66> [0,70]	0,44 (0,5D) <0,67> [0,71]	0,85 (0,) <0, > [0,]	0,86 (0,) <0, > [0,]		
~ 60(7E) (7E) Π	! 1 (21) <> [0,78]	@ 2 (22) <> [0,79]	# 3 (23) <> [0,7A]	\$ 4 (24) <> [0,7B]	% 5 (25) <> [0,7C]	^ 6 (26) <> [0,7D]	& 7 (27) <> [0,7E]	* 8 (28) <> [0,7F]	(9 (29) <> [0,80]) 0 (2A) <> [0,81]	- = (2B) <> [0,82]	+ = (2C) <> [0,83]	BackSpace 08(08) <F> Π	
Tab	Q 71(51) <11> [0,10]	W 77(57) <17> [0,11]	E 65(45) <05> [0,12]	R 72(52) <12> [0,13]	T 74(54) <14> [0,14]	Y 79(59) <19> [0,15]	I 75(55) <15> [0,16]	O 69(49) <0F> [0,17]	P 6F(4F) <0F> [0,18]	S 70(50) <10> [0,19]	B 5B(7B) <1B> [0,1A]	N 5D(7D) <1D> [0,1B]	Enter	
Caps Lock	A 61(41) <01> [0,1E]	S 73(53) <13> [0,1F]	D 64(44) <04> [0,20]	F 66(46) <06> [0,21]	G 67(47) <07> [0,22]	H 68(48) <08> [0,23]	J 6A(4A) <0A> [0,24]	K 6B(4B) <0B> [0,25]	L 6C(4C) <0C> [0,26]	;	3B(3A) 27(22) <> [0,27]	0D(0D) <0A> Π		
Shift	Z 7A(5A) <1A> [0,2C]	X 78(58) <18> [0,2D]	C 63(43) <03> [0,2E]	V 76(56) <16> [0,2F]	B 62(42) <02> [0,30]	N 6E(4E) <0E> [0,31]	M 6D(4D) <0D> [0,32]	<	>	2C(3C) 2E(3E) 2F(3F) <> [0,33]	?	Shift		
Ctrl	Alt	Macro	Space						Alt	Ctrl				
		0 <> Π				20(20) <20> [20]				5C(7C) <1C> Π				

Print	Scroll Lock	Pause
2A() <0,72> Π		0

Insert	Home	Page Up
0,52 () <>	0,47 () <>	0,49 () <>

Delete	End	Page Down
0,53 () <>	0,4F () <>	0,51 () <>

↑
0,48 () <>

←	↓	→
0,4B () <>	0,50 () <>	0,4D () <>

CODE (in)	LEGEND (Hexadecimal)
Extended Code-0,XX	Normal- XX
Alt-<XX>	Control-<XX>
	[XX]

Num Lock	/	*	-

7 Home	8 ↑	9 Pg Up
0,47 (37)	0,48 (38)	0,49 (39)
<0,77>	<0,84>	+

4 ←	5	6 →
0,4B (34)	0,4C (35)	0,4D (36)
<0,73>	<0,74>	

1 End	2 ↓	3 Pg Dn
0,4F (31)	0,50 (32)	0,51 (33)
<0,75>	<0,76>	Enter

Number "6₁₀" → "36_{hex}"
"36"=0011 0110

Letter "k" → "6B_{hex}"
"6B"=0110 1011

Character "+" → "2B_{hex}"
"2B"=0010 1011

Mistake: "=" equals "3D_{hex}" not "2B_{hex}"


Moore's Law

The law is named after Intel co-founder [Gordon E. Moore](#), who described the trend in his 1965 paper.

Moore's Law is the observation that, over the [history of computing hardware](#), the number of [transistors](#) on [integrated circuits](#) doubles about every two years.

Exponential Increase with Time

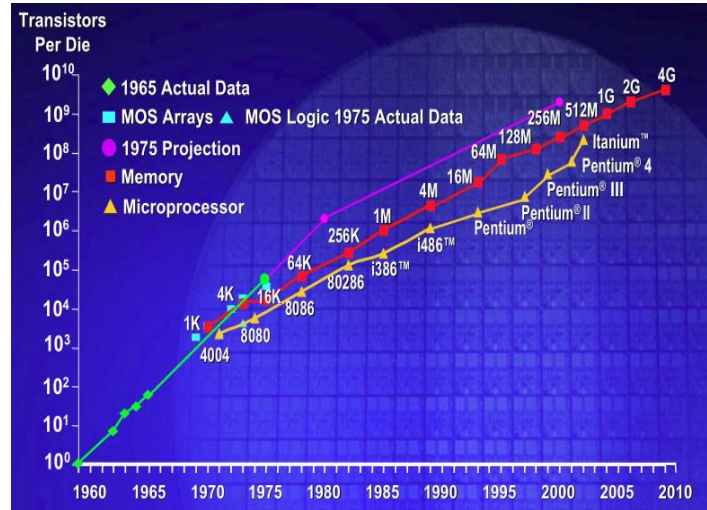- [memory capacity](#) (Moore to 1965)
- number of transistors, [processing speed](#)
- number and size of [pixels](#) in [cameras](#)



[Moore's Law Got Me!](#) **

(1:42, Mythbusters *)

[What is Moore's Law](#) ** (2:25, 2007)

[Moore's Law](#) (11:51)

Moore's Law – Computing Power (speed/\$1,000)

1 The accelerating pace of change ...



2 ... and exponential growth in computing power ...

Computer technology, shown here climbing dramatically by powers of 10, is now progressing more each hour than it did in its entire first 90 years

COMPUTER RANKINGS

By calculations per second per \$1,000



Analytical engine
Never fully built, Charles Babbage's invention was designed to solve computational and logical problems



Colossus
The electronic computer, with 1,500 vacuum tubes, helped the British crack German codes during WW II



UNIVAC I
The first commercially marketed computer, used to tabulate the U.S. Census, occupied 943 cu. ft.




Apple II
At a price of \$1,298, the compact machine was one of the first massively popular personal computers




Power Mac G4
The first personal computer to deliver more than 1 billion floating-point operations per second

3 ... will lead to the Singularity

 

Moore's Law – Computing Power/Cost

 

Questions?

Today – Pulsed Digital ICs

Electronic Clocks require pulsed ICs

- **Digital Watches** -
1 MHz crystal
divided down to 1 Hz
- **All Computers** –
need to **synchronize**
gate operations
(GHz)

Digital Pulsed ICs

- **One-Shot, Oscillator, Ch-23**
 - 74121 one-shot
 - 555 timer/oscillator
- **Flip-Flops, Ch-21**
 - RS flip-flops
 - D flip-flop (D latch)
 - T flip-flop
 - **JK flip-flop (toggle)**
- **Registers and Counters, Ch-24**
 - binary counter

Computer Speed – Clock Rate, Architecture, Cores

1980

Intel 8088

4.77 MHz



2000

1 GHz



Now

3+ GHz

Clock tic

0.3 nsec

300 psec

Clock Speed

Also called *clock rate*, the speed at which a microprocessor executes instructions.

Every [computer](#) contains an internal clock that regulates the rate at which instructions are executed and synchronizes all the various computer components.

The [CPU](#) (central processing unit) requires a fixed number of [clock ticks](#) (or *clock cycles*) to execute each instruction.

The faster the clock, the more instructions the CPU can execute.

The internal [architecture](#) of a CPU also effects a CPU's performance, so two different CPUs with the same clock speed will not necessarily perform equally.

Whereas an Intel 80286 (16-bit) microprocessor requires 20 cycles to multiply two numbers, an Intel 80486 (32-bit) performs the same calculation in a single clock tick. 20 times faster!

Also, increasing the number of “[cores](#)” operating in parallel increases computation speed. (dual core, quad core, etc.)

Measuring Computer Performance – IPS and FLOPS

Instructions per Second (IPS)

Computer performance can be measured in IPS or **MIPS (million IPS)**. Examples of **integer** operation include data movement (A to B) or value testing (If A = B, then C). MIPS as a performance benchmark is adequate when a computer is used in database queries, **word processing**, and **spreadsheets** (wiki).

2016 – Intel i7 CPU, 238,000 MIPS at 3.0 GHz
 > 200 billion instructions/second

FLOPS – better measure of performance

In computing, **FLOPS** (for **F**loating-point **O**perations **P**er **S**econd) is a measure of computer performance, useful in fields of **scientific calculations** that make heavy use of floating-point calculations. For such mathematical cases it is a more accurate measure than the generic IPS.

2017 – using 3 AMD commercial graphic cards (\$2,500)
 achieved 75 TFLOPS (~ 10^{14} operations/sec)

Floating point number
 e.g. 1.528535×10^{15}


20-40 IPS ~ 1 FLOPS

Computer performance

Name	FLOPS
yottaFLOPS	10^{24}
zettaFLOPS	10^{21}
exaFLOPS	10^{18}
petaFLOPS	10^{15}
teraFLOPS	10^{12}
gigaFLOPS	10^9
megaFLOPS	10^6
kiloFLOPS	10^3

Supercomputer Architecture


Supercomputers are “scalable”

 

2008 IBM Roadrunner
> 1 PFLOPS

19,000 processors, 296 computer racks
2.4 MW power, \$100M

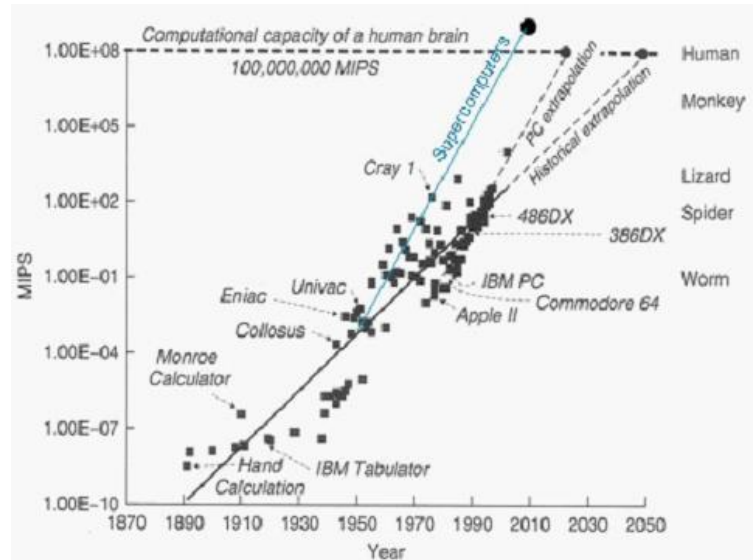2020 Fujitsu Fugaku, Japan
415 petaFLOPS (1E13 MIPS) →



Questions?

Pulsed ICs

We will now briefly cover the following pulsed ICs:

Multivibrators

- 74121 One-Shot
- 555 Timer/Oscillator



Flip-Flops

- **RS Flip-Flop**
- **D Flip-Flop**
- T Flip-Flop (toggle)
- **JK Flip-Flop** (universal)

74121 One-Shot

skip

  
Suppose you want to lengthen a pulse to a preset time.
 Example: Lengthen a 50 ns TTL pulse to light an LED.
 Turning on an LED for only 50 ns would be nearly invisible.
Stretch 50 ns → 1 s
74121 One-Shot
 Monostable Multivibrator



Input triggers:
A1, A2 – edge triggers
 B – level trigger
Q – output

$$\tau(s) = \ln(2) R(\Omega)C(F)$$

R=140 kΩ, C=10 μF
 $\tau = 1 s$

 

555 as Monostable Multivibrator (one-shot)

skip


555 as a One-Shot
 Use: lengthen a pulse to a preset time.
 Stretch 50 ns → 1 s

Trigger
 Trigger (pin 2) is pulled HIGH
 when the switch is closed


$$\tau(s) = \ln(3) R(\Omega)C(F) = 1.1RC$$

R=100 kΩ, C=10 μF
 $\tau = 1.1 \text{ s}$

555 Timer

 

8-Pin DIP

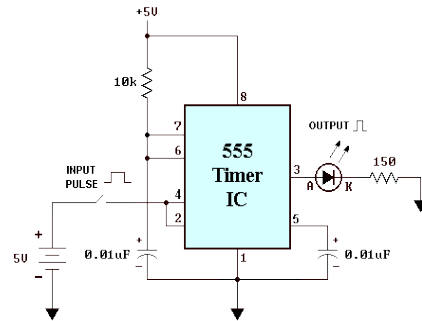

555 Timer as a Monostable Multivibrator

555 as Astable Multivibrator (oscillator)

skip

555 as an Oscillator

Triggers itself

C_1 charges up from $1/3 V_{cc}$ to $2/3 V_{cc}$

Charges to $t_1 = \ln(2) (R_1 + R_2) C_1$

At $2/3 V_{cc}$ discharge $t_2 = \ln(2) R_2 C_1$

On time: $t_1 = 0.693 (R_1 + R_2) C_1$



Off time: $t_2 = 0.693 R_2 C_1$

Period: $T = t_1 + t_2 = 0.693 (R_1 + 2R_2) C_1$

Frequency: $f = 1.44 / [(R_1 + 2R_2) C_1]$

Duty Cycle: on-time/period

$D = R_1 / (R_1 + 2R_2)$

  

Example

Flash an LED on for 0.1 s every second

For $t_{off} > t_{on}$, add diode across R_2

Then on time $= t_1 = 0.693 R_1 C$

Off time $= t_2 = 0.693 R_2 C$

For $C = 10 \mu\text{F}$

$R_1 = 14.4 \text{ k}\Omega$, $R_2 = 130 \text{ k}\Omega$

* Vary components in a running oscillator

[See 555 Tutorial](#)


Digital ICs that use Pulses

These include **Flip-Flops, Counters, and Displays**

Before, we had digital voltages that were more or less constant in time. When sending digital information, or performing computations, you need a train of digital pulses.





→ [Sequential Logic](#)

 Computers operate by performing logic operations (AND/OR/NOT) sequentially in time. There is a **clock-rate** that runs at GHz pulse rates. Thus, logic gate operations change several times every **nanosecond**. And 64 operations (*64-bit*) can be performed at one time ([Parallel Logic](#)).



Flip-Flop Types

    Flip-flops are heavily used for digital data **transfer** and **storage** and are commonly used in banks called "registers" for the storage of binary numerical data.



1 or 2 inputs

2 outputs

Q and \bar{Q}

See: [Flip-flop \(electronics\)](#) (wiki)

Flip-Flops

Why Flip-Flops?


Basic building block of all **memory**, counters, binary math

What is a Flip-Flop?

"Flip-flop" is the common name given to two-state devices which offer basic memory for [sequential logic](#) operations.

- **Two** outputs, two stable states
Outputs (Q , \bar{Q}), ($Q=1$ or 0)
- **Bistable Multivibrator**
Also called a **Latch**, pulse sets Q and it remains there

SR Flip-flop
(Set-Reset)

 

Basic data storage device. It holds data until reset.

RS Flip-Flop

S=Set → $Q=1$, $\bar{Q}=0$

R=Reset → $Q=0$, $\bar{Q}=1$


Set or reset the output Q

The first electronic flip-flop was invented in 1918 by [William Eccles](#) and [F. W. Jordan](#). It consisted of two active elements ([vacuum tubes](#)).

RS Flip-Flop

 Example: RS Flip-Flop

S=Set, R=Reset
 Uses **positive**-going pulses
 Contains 2 NORs



NOR - any **1** gives a **0**
0 and **0** gives a **1**

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

RS Flip-Flop with pulse input

R	S	new Q	new Q'	
0	0	nc	-	
0	1	1	0	set
1	0	0	1	reset
1	1	?	?	






nc=no change (last value)

Feedback wires maintain constant output values

[See how an RS FF switches](#) (wiki)

RS Flip-Flop

     NOR – (any **1** gives a **0**) – (**0** and **0** gives a **1**)



RS Flip-Flop with pulse input

R	S	new Q	new \bar{Q}	
0	0	nc	-	
0	1	1	0	set
1	0	0	1	reset
1	1	?	?	


nc=no change (last value)

Questions?

RS Flip-Flop

skip

 Example: RS Flip-Flop
S=Set, R=Reset
 Uses **negative-going pulses**
 Contains 2 NANDs



NAND - any 0 gives a 1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

RS Flip-Flop with pulse input


S	R	new Q	new Q'	
1	1	nc	-	
0	1	1	0	(set)
1	0	0	1	(reset)
0	0	?	?	

nc=no change (last value)

Summary: RS and RS Flip-Flops


RS Flip-Flop

 Uses **positive-going** pulses
 Contains 2 NORs
 Any 1 gives a 0



RS Flip-Flop

 Uses **negative-going** pulses
 Contains 2 NANDs
 Any 0 gives a 1



Don't get confused about the RS or RS notation.

RS refers to a positive-going pulse.

RS refers to a negative-going pulse.

Most people simply drop the (NOT) bars on R and S and assume either positive-going or negative-going pulses.

Questions?



Clocked Flip-Flop

Clock Pulse Notation
 Clock = CK = CLK = CP = Enable
 CLK, also called **Enable**

Clock pulse enables inputs

Nothing changes unless there is a clock pulse

  CLK = 0 → no change in outputs
 CLK = 1 → new RS changes output





Edge (rising) triggering

D Latch – Value Enabled

skip

  
D latch
 Only one input = **D**
 plus enable = **E**



The D Latch captures the value of the D-input whenever enable is on, E=1. That captured value becomes the Q output. At other times, the output Q does not change.

Value Enabled
 Depends on the value of E, not edge triggered.

Regular D-latch response

 

Value Enabled

[D-latch and Flip-Flop](#) (0-4:53, shows timing), 15:42

Clocked D Flip-Flop – Edge Triggered

By far the most important FF Stores one input (MEMORY)




Clocked D Flip-Flop
 Only one input = **D**
 plus clock pulse = **CLK**

The D flip-flop captures the value of the D-input at a definite portion of the clock cycle (such as the **rising edge** of the clock).

Edge Triggering

That captured value becomes the Q output. At other times, the output Q does not change.

   The D flip-flop can be viewed as a **memory cell**, a zero-order hold, or a delay line.



Edge triggering (rising)

* Watch: [D-latch and Flip-Flop](#) (11:20-12:10), 15:42

Enabling/Triggering Flip-Flops


skip

D Latch – value enabled


D Flip-Flop – edge triggered

Value Enabling

Regular D-latch response

 


Edge triggering

 

JK Flip-Flop

JK Flip-Flop

 
Most powerful
Can be configured as
RS-FF, D-FF, T-FF



JK Flip-Flop

J	K	CLK	Q _{next}	
0	0	↑	Q ₀	hold
1	0	↑	1	set
0	1	↑	0	reset
1	1	↑	Q ₀	toggle

OK →

 

T = toggle

The JK flip-flop augments the behavior of the SR flip-flop by interpreting **J=Set** and **K=Reset**.
Q₀ goes into Q_{next}

- The combination J=1, K=0 is a command to **set** the flip-flop (Q_{next}=1)
- The combination J=0, K=1 is a command to **reset** the flip-flop (Q_{next}=0)
- The combination J=K=1 is a command to **toggle** the flip-flop (Q₀ → Q₀)
On the CLK edge, Q₀ is set to Q_{next}=Q₀.

Q_{next} = J Q₀ + K Q₀

Watch: [JK and T Flip-Flop](#), (0-8:15) 13:09 *

Questions?

T Flip-Flop: TOGGLE

skip

Clocked T Flip-Flop: TOGGLE



Only one input = **T**
plus clock pulse = **CP**

If the T input is high, the T flip-flop changes state ("toggles") whenever the clock input is strobed.

Simply $Q \rightarrow \bar{Q}$

If the T input is low, the flip-flop holds the previous value.

This behavior is described by:
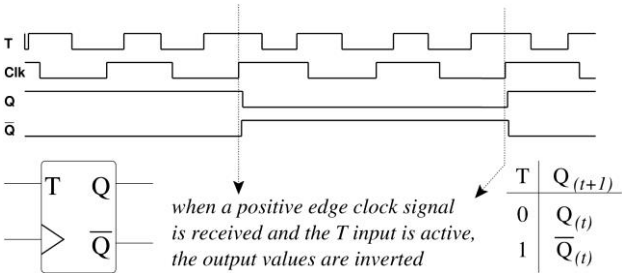 
$$Q_{next} = T \bar{Q} + \bar{T} Q$$


* Watch: [JK and T Flip-Flop](#), (8:15+) 13:09



Toggle from JK Flip-Flop

Make JK-FF into
simple **Toggle**

Set J=K=1

Each time a clock pulse edge comes,
the output is toggled.

Q → \bar{Q} → Q → \bar{Q} → Q →

  

Use toggle from JK flip-flop
as a **binary counter**

Frequency is $\frac{1}{2}$
 $f \rightarrow f/2$

Questions?

Binary Counter, Ch. 24

Binary Counter

Counts how many clock pulses come by



Use the JK-FF in **TOGGLE** mode

Binary Number DCBA

D	C	B	A
2^3	2^2	2^1	2^0
8	4	2	1
Q_2	Q_1	Q_0	CLK
FF2	FF1	FF0	CLK

Note:

  “A” is the least significant bit in DCBA
(e.g. 0101)





* Watch: [Binary Counter](#), 20 sec

See [Binary Counter](#) details, 10 min

Lab-8b


Flip-Flop, Counters, Displays

 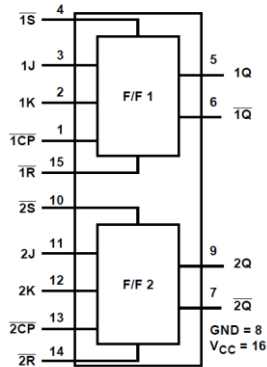- Design and construct a binary counter circuit using JK flip-flops
- The circuit cycles through the binary numbers 000-111
- Convert binary numbers to BCD
- Light LED digital number display




Lab-8b, Roll the Dice

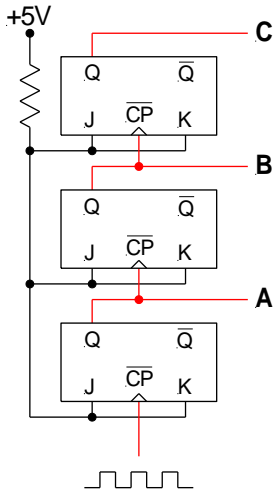Make 4-bit Counter
Three [74112](#) JK-FF



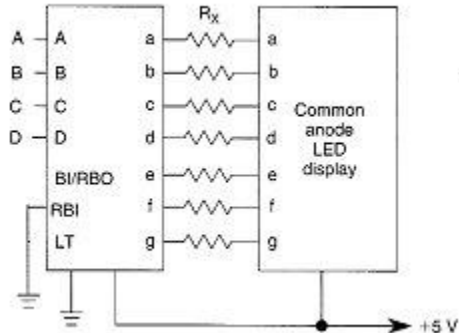[SN74LS47N](#)
BCD-to-seven-segment
common anode
decoder/driver



$R_x = 200-500 \Omega$

[LTS-4801B](#)

7-segment LED
for digits 0-9
common anode



See [Decoder/Display](#)

Note: "A" is the least significant bit (CBA)

Wednesday EXAM-2, Nov 18

Magneto-electronics
Optoelectronics
Digital Electronics
Pulsed ICs

Due Wed, Nov 18

Homework Ch. 21
Lab-8a and 8b in **one** report

mwisho